

CE-321L/CS-330L: Computer Architecture

Project Report

**Building a 5-stage pipelined processor
capable of executing any one array sorting
algorithm**

Huzaifa Riaz - 07741

Humayun Hasan - 06527

Mohammed Haider Abbas - 06418

27-April-2023

Introduction:

The primary objective of this project is to build a 5-stage pipelined processor capable of executing any one array sorting algorithm. This project aims to convert an existing lab 11 single-cycle processor architecture to a pipelined one with minor modifications to the circuit. The project involves implementing the bgt or blt instruction to swap two values. The project is divided into three parts, and the recommended course of action involves choosing a suitable sorting algorithm, converting its pseudocode to assembly using the RISC-V instruction set, and testing its working on the assembly code simulator. In part two, the existing processor is modified to make it a pipelined one (5 stages), and each instruction is tested separately to ensure that the pipelined processor version can execute one instruction correctly in isolation. In part three, circuitry is introduced to detect hazards (data, control, and structural if needed) and handle them in hardware using forwarding, stalling, and flushing the pipeline. By completing all three parts of this project, the array sorting code should be able to function correctly on the pipelined processor architecture.

Task 1 - Single Cycle Processor With Bubble Sort

Sort Used – Bubble sort:

C code for bubble sort

```
void bubbleSort(int arr[], int n) {  
    int i, j;  
    for (i = 0; i < n-1; i++) {  
        for (j = 0; j < n-i-1; j++) {  
            if (arr[j] > arr[j+1]) {  
                int temp = arr[j];  
                arr[j] = arr[j+1];  
                arr[j+1] = temp;  
            }  
        }  
    }  
}
```

We used bubble sort as our choice of sort mainly because of two reasons.

1. Simplicity: Bubble sort is one of the simplest sorting algorithms to understand and implement. It only requires a few lines of code, making it easy to implement and debug.
2. Small data sets: Bubble sort has a time complexity of $O(n^2)$, which means that for small data sets, bubble sort can be faster than more complex algorithms because it has a small constant factor.

Bubble Sort Assembly Code

$x22 = i$, $x23 = j$, $x28 = \text{address}_i$, $x29 = \text{address}_j$, $x5 = \text{temp}$, $x8 = 5$

```

Loop1 :
blt x22 , x8 , Loop2      # i < 5
beq x0 , x0 , Exit

Loop2 :
addi x23 , x22 , 0        # j = i
addi x29 , x28 , 0        # address_j = address_i # j
blt x23 , x8 ,            # j < 5
Loop3 beq x0 , x0 ,
Loop1
Loop3 :
ld x12 , 0( x28 )         # x12 = a[ i]
ld x13 , 0( x29 )         # x13 = a[ j]
blt x12 , x13 , if
addi x23 , x23 , 1        # j++
addi x29 , x29 , 8        # address_j +=8 #
blt x23 , x8 ,            # j < 8
Loop3 addi x22 ,          # i++
x22 , 1 addi x28 ,        # address_i +=8
x28 , 8 beq x0 , x0
if:
add x5 , x12 , x0         # temp = a[ i]
sd x13 , 0( x28 )         # a[ i] = a[ j]
sd x5 , 0( x29 )          # a[ j] = temp
addi x23 , x23 , 1        # j++
addi x29 , x29 , 8        # address_j +=8 #
blt x23 , x8 ,            # j < 8
Loop3 addi x22 ,          # i++
x22 , 1 addi x28 ,        # address_i +=8
x28 , 8 beq x0 , x0
Loop1
Exit :

```

Changes to Lab 11 – Single Cycle Processor For blt Instruction

Control Unit:

```
43         end
44     7'b0010011: //addi
45     begin
46         ALUSrc  = 1'b1;
47         MemtoReg = 1'b0;
48         RegWrite = 1'b1;
49         MemRead  = 1'b0;
50         MemWrite = 1'b0;
51         Branch   = 1'b0;
52         ALUOp    = 2'b00;
53     end
54     7'b1100011: // SB- type (beq/blt)
55     begin
56         ALUSrc  = 1'b0;
57         MemtoReg = 1'bx;
58         RegWrite = 1'b0;
59         MemRead  = 1'b0;
60         MemWrite = 1'b0;
61         Branch   = 1'b1;
62         ALUOp    = 2'b01;
63     end
64
65     default:
66     begin
67         ALUSrc  = 1'b0;
68         MemtoReg = 1'b0;
69         RegWrite = 1'b0;
70         MemRead  = 1'b0;
71         MemWrite = 1'b0;
72         Branch   = 1'b0;
73         ALUOp    = 2'b00;
74     end
75 endcase
76 end
77
```

- SB-type (beq/blt)

ALU Control:

```
7
8  always @(*)
9  begin
10     case(ALUOp)
11     2'b00:
12     begin
13         Operation = 4'b0010;
14     end
15     2'b01:                                     // branch type instructions
16     begin
17         case(Funct[2:0])
18         3'b000:                                 // beq
19         begin
20             Operation = 4'b0110; // subtract
21         end
22         3'b100:                                 // blt
23         begin
24             Operation = 4'b0100; // less than operation
25         end
26         endcase
27     end
28
29     2'b10:
30     begin
31         case(Funct)
32         4'b0000:
33         begin
34             Operation = 4'b0010;
35         end
36         4'b1000:
37         begin
38             Operation = 4'b0110;
39         end
40         4'b0111:
41         begin
42             Operation = 4'b0000;
43         end
44         4'b0110:
45         begin
46
```

- Modified the ALU Control that generates the 4-bit ALU Control input.
- The Control Unit takes as input the Func Field [1-bit from funct7 field (bit 30) + 3-bit funct3 field (bits 14:12)] and a 2-bit control field which we call ALUOp. The output is a 4-bit signal (determined by Func and ALUOp field) that directly controls the ALU by generating one of six operations to be performed in our case.
- ALUOp indicates whether the operation to be performed should be add (00)

for loads and stores, or be determined by the operation encoded in the funct7 and funct3 fields (10, 01). We added an additional case structure when ALUOp was '01' i.e. when there was a branch type instruction. We checked for two types under that. Lines 14 - 26:

1. Beq instruction (tests for equality): When Func field's least three significant bits were '000' (i.e. when func3 field was '000'), we would require a subtract operation to subtract and test if equals 0 and so subtract operation was assigned.
2. Blt instruction (tests for lesser than): When Func field's least three significant bits were '100' (i.e. when func3 field was '100'), we would require a check less than operation and so less than operation was assigned.

ALU:

```

1 module ALU(a,b,ALUop,Result,Zero);
2   input [63:0] a, b;
3   input [3:0] ALUop;
4   output reg [63:0] Result;
5   output Zero;
6
7
8
9   always@(a or b or ALUop)
10     begin
11       case (ALUop)
12         4'b0000: Result = a & b;           // AND
13         4'b0001: Result = a | b;           // OR
14         4'b0010: Result = a + b;           // Addition
15         4'b0110: Result = a - b;           // Subtraction
16         4'b1100: Result = ~(a | b);        // Nor
17         4'b0100: Result = (a < b)? 0: 1;    // Lesser than
18       endcase
19     end
20   assign Zero =(Result==0); //equal or <
21
22
23 endmodule

```

- Modified to add lesser than
- If first value is lesser than the second value, then '0' is assigned to Result. If Result == 0 then just like the beq instruction, '0' would be assigned to Zero .

With this, no additional changes in the hardware are required to check for an additional branch type instruction.

Changes To Lab 11 - For Running Bubble Sort

Instruction Memory:

Major changes were made in Instruction memory where each instruction of assembly code was converted into 32 bit binary address, broken down and passed to InstMemory as 8 bits.

```
module InstructionMemory(Inst_Address,Instruction);
  input [63:0] Inst_Address;
  output reg [31:0]Instruction;
  reg [7:0] InstMemory [95:0];
  integer i;

  initial
    begin
      //blt x22, x8,8
      InstMemory[0] = 8'b01100011;
      InstMemory[1] = 8'b01000100;
      InstMemory[2] = 8'b10001011;
      InstMemory[3] = 8'b0;

      //beq x0,x0,92
```

```

InstMemory[4] = 8'b01100011;
InstMemory[5] = 8'b00001110;
InstMemory[6] = 8'b00000000;
InstMemory[7] = 8'b00000100;

//addi x23,x22,0
InstMemory[8] = 8'b10010011;
InstMemory[9] = 8'b00001011;
InstMemory[10] = 8'b00001011;
InstMemory[11] = 8'b0;

//addi x29,x28,0
InstMemory[12] = 8'b10010011;
InstMemory[13] = 8'b00001110;
InstMemory[14] = 8'b00001110;
InstMemory[15] = 8'b0;

//blt x23,x8,Loop3
InstMemory[16] = 8'b01100011;
InstMemory[17] = 8'b11000100;
InstMemory[18] = 8'b10001011;
InstMemory[19] = 8'b0;

//beq x0,x0, Loop1
InstMemory[20] = 8'b11100011;
InstMemory[21] = 8'b00000110;
InstMemory[22] = 8'b00000000;
InstMemory[23] = 8'b11111110;

//ld x12, 0(x28) - x12 = a[i]
InstMemory[24] = 8'b00000011;
InstMemory[25] = 8'b00110110;
InstMemory[26] = 8'b00001110;
InstMemory[27] = 8'b00000000;

```



```
//ld x13, 0(x29) - x13 = a[j]
InstMemory[28]=8'b10000011;
InstMemory[29]=8'b10110110;
InstMemory[30]=8'b00001110;
InstMemory[31]=8'b00000000;
```

```
//blt x12,x13,if
InstMemory[32]=8'b01100011;
InstMemory[33]=8'b01001110;
InstMemory[34]=8'b11010110;
InstMemory[35]=8'b00000000;
```

```
//addi x23,x23,1 - j++
InstMemory[36]=8'b10010011;
InstMemory[37]=8'b10001011;
InstMemory[38]=8'b00011011;
InstMemory[39]=8'b00000000;
```

```
//addi x29,x29,8 - locj+= 8
InstMemory[40]=8'b10010011;
InstMemory[41]=8'b10001110;
InstMemory[42]=8'b10001110;
InstMemory[43]=8'b00000000;
```

```
//blt x23,x8,Loop3
InstMemory[44]=8'b11100011;
InstMemory[45]=8'b11000110;
InstMemory[46]=8'b10001011;
InstMemory[47]=8'b11111110;
```

```

//addi x22,x22,1 #i++
InstMemory[48]=8'b00010011;
InstMemory[49]=8'b00001011;
InstMemory[50]=8'b00011011;
InstMemory[51]=8'b00000000;

//addi x28, x28,8 - loci+=8
InstMemory[52]=8'b00010011;
InstMemory[53]=8'b00001110;
InstMemory[54]=8'b10001110;
InstMemory[55]=8'b0;

//beq x0,x0,Loop1
InstMemory[56]=8'b11100011;
InstMemory[57]=8'b00000100;
InstMemory[58]=8'b00000000;
InstMemory[59]=8'b11111100;

//add x5,x12,x0 # temp = a[i]
InstMemory[60]=8'b10110011;
InstMemory[61]=8'b00000010;
InstMemory[62]=8'b00000110;
InstMemory[63]=8'b0;

//sd x13, 0(x28) #a[i] = a[j]
InstMemory[64]=8'b00100011;
InstMemory[65]=8'b00110000;
InstMemory[66]=8'b11011110;
InstMemory[67]=8'b0;

//sd x5, 0(x29) -a[j] = temp
InstMemory[68]=8'b00100011;
InstMemory[69]=8'b10110000;
InstMemory[70]=8'b01011110;

```

```
InstMemory[71]=8'b0;
```

```
    //addi x23,x23,1 - j++  
InstMemory[72]=8'b10010011;  
InstMemory[73]=8'b10001011;  
InstMemory[74]=8'b00011011;  
InstMemory[75]=8'b0;
```

```
    //addi x29,x29,8 - locj+= 8  
InstMemory[76]=8'b10010011;  
InstMemory[77]=8'b10001110;  
InstMemory[78]=8'b10001110;  
InstMemory[79]=8'b00000000;
```

```
    //blt x23,x8,Loop3:  
InstMemory[80]=8'b11100011;  
InstMemory[81]=8'b11000100;  
InstMemory[82]=8'b10001011;  
InstMemory[83]=8'b11111100;
```

```
    //addi x22,x22,1 - i++  
InstMemory[84]=8'b00010011;  
InstMemory[85]=8'b00001011;  
InstMemory[86]=8'b00011011;  
InstMemory[87]=8'b0;
```

```
    //addi x28, x28,8 - loci+=8  
InstMemory[88]=8'b00010011;  
InstMemory[89]=8'b00001110;  
InstMemory[90]=8'b10001110;  
InstMemory[91]=8'b0;
```

```
    //beq x0,x0,Loop1
```

```

    InstMemory[92]=8'b11100011;
    InstMemory[93]=8'b00000010;
    InstMemory[94]=8'b00000000;
    InstMemory[95]=8'b11111010;

    end
    always @(Inst_Address)
    begin
        Instruction = {InstMemory[Inst_Address + 3], InstMemory[Inst_Address +
2],InstMemory[Inst_Address + 1], InstMemory[Inst_Address]} ;
    end

endmodule

```

Register Files:

```

4
5     initial
6     begin
7         for (i = 0; i < 32; i = i + 1)
8         begin
9             Registers[i] = 0;
10        end
11        Registers[8] = 5;
12
13

```

- Assigned the 8th register (x8) the value 5 ie number the elements we'll be sorting in bubble sort and all the other registers are assigned the value 0.


Data Memory:

```

initial
begin
    for (i = 0; i < 64; i = i + 1)
    begin
        DataMemory[i] = 0;
    end
    DataMemory[0]  = 8'd2;
    DataMemory[8]  = 8'd1;
    DataMemory[16] = 8'd3;
    DataMemory[24] = 8'd0;
    DataMemory[32] = 8'd4;

```

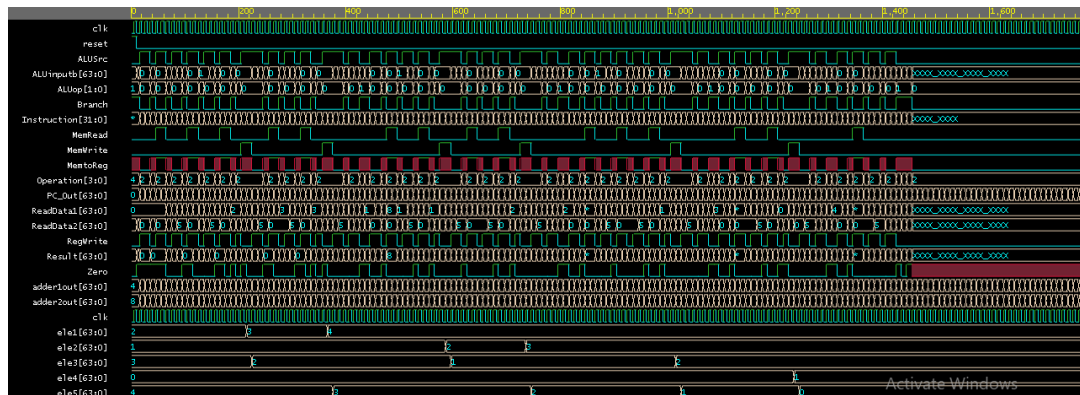- Passed 2,1,3,0,4 in the data memory for sorting to be applied on them
- If the sorting works properly it should be sorted as 4,3,2,1,0



Full wave



Sorting on single cycle processor in working condition

EDA link for viewing detailed wave = <https://www.edaplayground.com/x/wdjz>

Task 2 - Introducing Pipelining


The first part of the discussion presented a single cycle processor capable of running Bubble sort. However, this type of implementation executes one instruction at a time, leading to inefficiency and wasted processing power. To address this, pipelining is introduced to enable the execution of multiple instructions simultaneously, depending on the number of stages in the pipeline. In a five-stage pipeline, different components of the processor work on different parts of multiple instructions at the same time. This allows the processor to work on up to five instructions simultaneously, increasing efficiency and reducing wasted processing power.

The processor implemented is divided in the following 5 stages:

- **IF** : Instruction Fetch
- **ID** : Instruction decode
- **EX** : Execution
- **MEM** : Data memory
- **WB** : Write back

Prior to diving into the specifics of each stage, its function, and discussing the Verilog implementation, let's take a look at the overall concept that we are aiming to implement.

This can be visualized through the following figure:

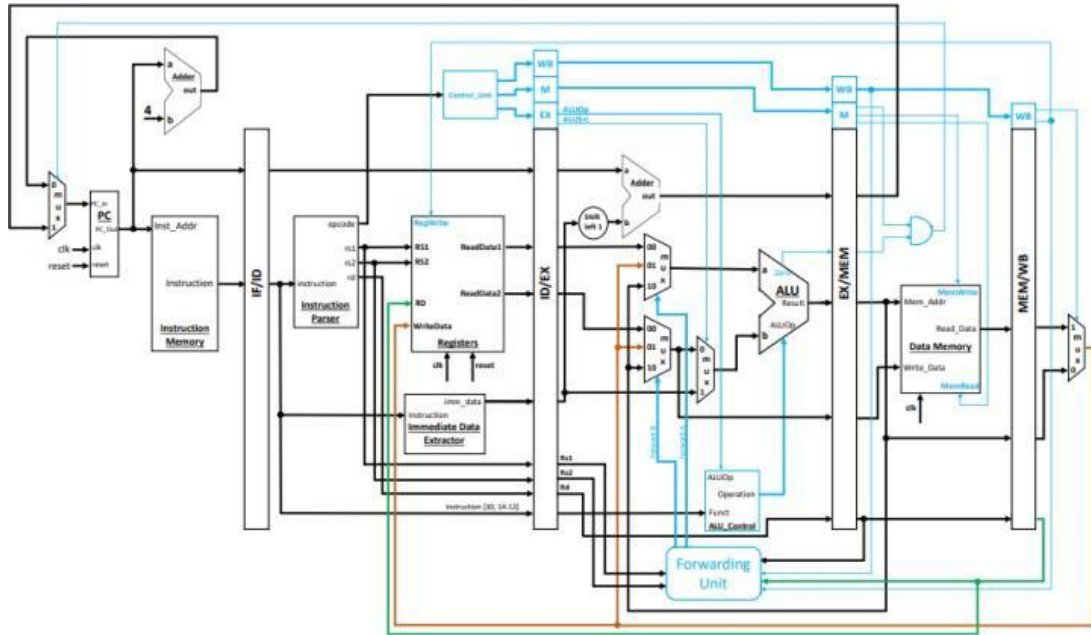

Stage 1 - Instruction Fetch (IF):

It is the first stage of our processor, which is located on the left side of the figure. It is responsible for fetching the instruction from memory. It accomplishes this by calculating the instruction's address using the program counter (PC) and accessing the instruction memory module. The fetched instruction is then sent to the next stage through the IF/ID register. Additionally, this stage handles jump addresses in the event that the previous instruction was a branch instruction. It does so by receiving the offset from the EX/MEM register.

```

1 module IFID
2 (
3     input clk,
4     input reset,
5     input [31:0] instruction,
6     input [63:0] A, //a
7     input flush,
8     input IFIDWrite,
9     output reg [31:0] inst,//instruction out,
10    output reg [63:0] a_out
11 );
12 always @(posedge clk)
13 begin
14     if (reset == 1'b1 || flush == 1'b1)
15     begin
16         inst = 32'b0;
17         a_out = 64'b0;
18     end
19     else if (IFIDWrite == 1'b0)
20     begin
21         inst = instruction;
22         a_out = A;
23     end
24 end
25 endmodule

```

The outputs from this stage are the intermediate connections between the Instruction Fetch and the Instruction decode stage.

Stage 2 - Instruction Decode (ID):

In the pipeline, this stage follows the initial stage of instruction fetching and is responsible for decoding instructions and performing register reads or writes. It starts by receiving the instruction fetched by the IF stage and proceeds to extract the relevant information.

After the instruction is fetched in the initial stage, it is passed on to the second stage of our pipeline where it undergoes decoding using the Instruction Parser and Data Extractor module. This enables us to determine the opcode, rd, rs1, and rs2 of the 32-bit instruction.

Following this, the RegisterFile module reads the contents of the relevant registers or writes back to them as necessary, with signals from the MEM/WEB register used

to determine whether it is a read or write operation. The Control Unit plays a crucial role in this stage, utilizing the opcode to forward signals to control the ALU and other operations in the processor.

Throughout this process, the flow of the program is maintained as signals are forwarded from right to left. Finally, all intermediate wire contents from the IF/ID stage are transmitted to the ID/EX stage.

```
1 module IDEX(SV/Veri
2   input clk,reset,
3   input [3:0] funct4_in,//funct4 of instruction from instruction memory
4   input [63:0] A_in,//adder input, output of IFID carried forward
5   input [63:0] readdata1_in, //from regwrite
6   input [63:0] readdata2_in, //from regwrite
7   input [63:0] imm_data_in, //from data extractor
8   input [4:0] rs1_in, //from instruction parser
9   input [4:0] rs2_in, //from instruction parser
10  input [4:0] rd_in, //from instruction parser
11  input branch_in,memread_in,memtoreg_in,memwrite_in,aluSrc_in,regwrite_in, //from control unit
12  input [1:0] Aluop_in,
13  input flush,
14  output reg [63:0] a,
15  output reg [4:0] rs1,
16  output reg [4:0] rs2,
17  output reg [4:0] rd,
18  output reg [63:0] imm_data,
19  output reg [63:0] readdata1, //2bit mux
20  output reg [63:0] readdata2, //2bit mux
21  output reg [3:0] funct4_out,
22  output reg Branch,Memread,Memtoreg, Memwrite, Regwrite,Alusrc,
23  output reg [1:0] aluop
24 );
```

```

25
26 always @ (posedge clk)
27 begin
28     if (reset == 1'b1 || flush == 1'b1)
29     begin
30         a = 64'b0;
31         rs1 = 5'b0;
32         rs2 = 5'b0;
33         rd = 5'b0;
34         imm_data = 64'b0;
35         readdata1 = 64'b0;
36         readdata2 = 64'b0;
37         funct4_out = 4'b0;
38         Branch = 1'b0;
39         Memread = 1'b0;
40         Memtoreg = 1'b0;
41         Memwrite = 1'b0;
42         Regwrite = 1'b0;
43         Alusrc = 1'b0;
44         aluop = 2'b0;
45     end
46     else
47     begin
48         a = A_in;
49         rs1 = rs1_in;
50         rs2 = rs2_in;
51         rd = rd_in;
52         imm_data = imm_data_in;
53         readdata1 = readdata1_in;
54         readdata2 = readdata2_in;
55         funct4_out = funct4_in;
56         Branch = branch_in;
57         Memread = memread_in;
58         Memtoreg = memtoreg_in;
59         Memwrite = memwrite_in;
60         Regwrite = regwrite_in;
61         Alusrc = aluSrc_in;
62         aluop = Aluop_in;
63     end
64 end
65 end
66 endmodule

```

Stage 3 - Execution:

Here all the calculations take place. This stage is responsible for two main tasks:

1. If the instruction is a branch instruction, then the offset value to be added to find the address of the next location is calculated by adder.
2. The ALU resides here, so all the operations are executed here.

After receiving the instruction from the IF stage, the Instruction Decode register provides the '**aluop**', which serves as the control signal for the ALU. The data to be written to the registers is determined by two MUX, but we will cover this in our

discussion of the Forwarding Unit and data hazard handling. For now, let's focus on the Execution stage and its role. Once all necessary calculations are completed, the Execution stage sends both the control signals obtained from the ID/EX stage and the calculated values to the Memory stage through the EX/MEM stage.

```

2 module EXMEM(
3   input clk,reset,
4   input [63:0] Adder_out, //output adder
5   input [63:0] Result_in_alu, //output 64bit alu
6   input Zero_in, //output 64bit alu
7   input [63:0] writedata_in, //output 2 bit mux2by1
8   input [4:0] Rd_in, //output IDEX
9   input branch_in,memread_in,mentoreg_in,memwrite_in,regwrite_in, //outputs IDEX
10  input flush,
11  input addermuxselect_in,
12  output reg [63:0] Adderout,
13  output reg zero,
14  output reg [63:0] result_out_alu,
15  output reg [63:0] writedata_out,
16  output reg [4:0] rd,
17  output reg Branch,Memread,Mentoreg, Memwrite, Regwrite,
18  output reg addermuxselect);
19
20  always @ (posedge clk)
21  begin
22    if (reset == 1'b1 || flush == 1'b1)
23    begin
24      Adderout = 64'b0;
25      zero = 1'b0;
26      result_out_alu = 63'b0;
27      writedata_out = 64'b0;
28      rd = 5'b0;
29      Branch = 1'b0;
30      Memread = 1'b0;
31      Mentoreg = 1'b0;
32      Memwrite = 1'b0;
33      Regwrite = 1'b0;
34      addermuxselect = 1'b0;
35    end
36    else
37    begin
38      Adderout = Adder_out;
39      zero = Zero_in;
40      result_out_alu = Result_in_alu;
41      writedata_out = writedata_in;
42      rd = Rd_in;
43      Branch = branch_in;
44      Memread = memread_in;
45      Mentoreg = mentoreg_in;
46      Memwrite = memwrite_in;
47      Regwrite = regwrite_in;
48      addermuxselect = addermuxselect_in;
49    end
50  end
51 endmodule

```

Stage 4 - Memory Access

Only Data Memory module is present in this stage, but this stage also sends signals back and forth. It checks whether the MemRead or MemWrite signals are high, and then performs the corresponding operation while setting the necessary control lines to write data to or read data from memory.

Additionally, it sends the register contents to the Execution stage for calculations to handle data hazards. The main objective of this register is to write data to memory if the MemWrite signal is high and read data from memory into the designated register if the MemRead signal is high. Finally, it transmits the contents of the registers and other control signals to the last stage of the pipeline through the MEM/WB register.

```

2 module MEMWB(
3     input clk,reset,
4     input [63:0] read_data_in,
5     input [63:0] result_alu_in, //2 bit 2by1 mux input b
6     input [4:0]Rd_in, //EX MEM output
7     input memtoreg_in, regwrite_in, //ex mem output as mem wb inputs
8     output reg [63:0] readdata, //1bit
9     output reg [63:0] result_alu_out, //1bit
10    output reg [4:0] rd,
11    output reg Memtoreg, Regwrite
12 );
13
14    always @(posedge clk)
15        begin
16            if (reset == 1'b1)
17                begin
18                    readdata = 63'b0;
19                    result_alu_out = 63'b0;
20                    rd = 5'b0;
21                    Memtoreg = 1'b0;
22                    Regwrite = 1'b0;
23                end
24            else
25                begin
26                    readdata = read_data_in;
27                    result_alu_out = result_alu_in;
28                    rd = Rd_in;
29                    Memtoreg = memtoreg_in;
30                    Regwrite = regwrite_in;
31                end
32            end
33        end
34    endmodule

```

Stage 5 - Write Back

This is the final stage of the processor, the right most part of the figure.

MemtoReg and RegWrite are the two control lines, MemtoReg decides between sending the ALU result or the register value and RegWrite, writes the chosen value to the register. This then is sent back to the ID stage to the registerfile so the contents of registers can be written back.

Forwarding Unit:

To address data hazards, we utilize techniques like stalling and forwarding. Of the two, forwarding is more effective and is the method we employ in our processor. Forwarding allows the value calculated in the execution stage to be directly sent to the ID stage when it's needed, without having to wait for it to be loaded into a register and then read from there.

```

1 module ForwardingUnit
2 (
3     input [4:0] RS_1, //ID/EX.RegisterRs1
4     input [4:0] RS_2, //ID/EX.RegisterRs2
5     input [4:0] rdMem, //EX/MEM.RegisterRd
6     input [4:0] rdwb, //MEM/WB.RegisterRd
7
8     input regwrite_wb, //MEM/WB.Regwrite
9     input regwrite_Mem, //EX/MEM.Regwrite
10    output reg [1:0] Forward_A,
11    output reg [1:0] Forward_B
12 );
13
14 always @(*)
15 begin
16     if ( (rdMem == RS_1) & (regwrite_Mem != 0 & rdMem != 0) )
17     begin
18         Forward_A = 2'b10;
19     end
20     else
21     begin
22         // Not condition for MEM hazard
23         if ( (rdwb == RS_1) & (regwrite_wb != 0 & rdwb != 0) & ~((rdMem == RS_1) & (regwrite_Mem != 0 &
24 rdMem != 0) ) )
25         begin
26             Forward_A = 2'b01;
27         end
28         else
29         begin
30             Forward_A = 2'b00;
31         end
32     end
33
34     if ( (rdMem == RS_2) & (regwrite_Mem != 0 & rdMem != 0) )
35     begin
36         Forward_B = 2'b10;
37     end
38     else
39     begin
40         // Not condition for MEM Hazard
41         if ( (rdwb == RS_2) & (regwrite_wb != 0 & rdwb != 0) & ~((regwrite_Mem != 0 & rdMem != 0) &
42 (rdMem == RS_2) ) )
43         begin
44             Forward_B = 2'b01;
45         end
46         else
47         begin
48             Forward_B = 2'b00;
49         end
50     end
51 end
52 endmodule

```

Task 3 - Flushing and Stalling

We have implemented Hazard detection, forwarding and flushing in our pipelined processor. Forwarding is used to pass data between instructions to avoid data hazards, stalling is used to resolve hazards that cannot be avoided through forwarding, and flushing is used to discard instructions in the pipeline when a hazard is detected to avoid stalls.

Hazard Detection:

```
module hazard_detection_unit
(
    input Memread,
    input [31:0] inst,
    input [4:0] Rd,
    output reg stall
);

initial
begin
    stall = 1'b0;
end

always @(*)
begin
    if (Memread == 1'b1 && ((Rd == inst[19:15]) || (Rd == inst[24:20])))
        stall = 1'b1;
    else
        stall = 1'b0;
    end
endmodule
```

This hazard detection unit detects RAW hazards by checking whether a memory read operation is being performed and whether the destination register for the current instruction matches the source register for a previous instruction. If a hazard is detected, the unit sets the stall signal to 1, indicating that the pipeline should be stalled until the hazard is resolved.

Flush:

This pipeline flush module detects branch instructions by checking whether the branch signal is 1. If a branch instruction is detected, the module sets the flush signal to 1, indicating that the pipeline should be flushed to prevent the execution of instructions that are no longer valid.

```
module pipeline_flush
(
    input branch,
    output reg flush
);

initial
begin
    flush = 1'b0;
end

always @(*)
begin
    if (branch == 1'b1)
        flush = 1'b1;
    else
        flush = 1'b0;
    end
endmodule
```

Forwarding:

Explained above as well, but to elaborate further more for its role with respect to task 3.

The code checks for two types of data hazards:

1. MEM Hazard: When the register destination of the memory stage (rdMem) matches the first or second source register of the current stage (RS_1 or RS_2) and there is a register write (regWrite_Mem=1), then data forwarding is required. The code sets Forward_A or Forward_B to 2'b10 to forward the data from the memory stage.
2. WB Hazard: When the register destination of the write-back stage (rdWb) matches the first or second source register of the current stage (RS_1 or RS_2) and there is a register write (regWrite_Wb=1), then data forwarding is required. The code sets Forward_A or Forward_B to 2'b01 to forward the

data from the write-back stage.

This Forwarding Unit module detects data hazards in the pipeline and forwards data from previous pipeline stages to the current stage to avoid stalling the pipeline. It does so by checking the destination register of each stage (rdMem and rdWb) and comparing it to the source registers of the current stage (RS_1 and RS_2). Depending on the hazard detected, the module sets Forward_A and Forward_B signals to forward the data from the appropriate stage.

```
1 module ForwardingUnit
2 (
3   input [4:0] RS_1, //ID/EX.RegisterRs1
4   input [4:0] RS_2, //ID/EX.RegisterRs2
5   input [4:0] rdMem, //EX/MEM.Register Rd
6   input [4:0] rdWb, //MEM/WB.RegisterRd
7
8   input regWrite_Wb, //MEM/WB.RegWrite
9   input regWrite_Mem, // EX/MEM.RegWrite
10  output reg [1:0] Forward_A,
11  output reg [1:0] Forward_B
12 );
13
14 always @(*)
15 begin
16   if ( (rdMem == RS_1) & (regWrite_Mem != 0 & rdMem != 0) )
17   begin
18     Forward_A = 2'b10;
19   end
20   else
21   begin
22     // Not condition for MEM hazard
23     if ( (rdWb == RS_1) & (regWrite_Wb != 0 & rdWb != 0) & ~((rdMem
24 == RS_1) & (regWrite_Mem != 0 & rdMem != 0) ) )
25     begin
26       Forward_A = 2'b01;
27     end
28     else
29     begin
30       Forward_A = 2'b00;
31     end
32   end
33
34   if ( (rdMem == RS_2) & (regWrite_Mem != 0 & rdMem != 0) )
35   begin
36     Forward_B = 2'b10;
37   end
38   else
39   begin
```



```

38         begin
39             // Not condition for MEM Hazard
40             if ( (rdWb == RS_2) & (regWrite_Wb != 0 & rdWb != 0) & ~
((regWrite_Mem != 0 & rdMem != 0) & (rdMem == RS_2) ) )
41                 begin
42                     Forward_B = 2'b01;
43                 end
44             else
45                 begin
46                     Forward_B = 2'b00;
47                 end
48             end
49         end
50     endmodule

```


Testing Flush signals and stall signals:

In order to ensure the proper functioning of the hazard detection unit and stall mechanism, a series of tests were carried out on the pipelined processor. These tests were designed to simulate different types of hazards that can occur in the pipeline and verify that the hazard detection unit is able to detect these hazards and stall the pipeline when necessary.

The first set of tests focused on data hazards, where a dependent instruction tries to read a register that has not been written to yet by the previous instruction. To simulate this, a series of instructions were loaded into the pipeline, where the second instruction tried to read from a register that was written to by the first instruction. The hazard detection unit was expected to detect this hazard and stall the pipeline until the first instruction had finished writing to the register.

The second set of tests focused on control hazards, where a branch instruction is executed and the pipeline needs to be flushed. To simulate this, a series of instructions were loaded into the pipeline, and a branch instruction was inserted in the middle. The hazard detection unit was expected to detect the branch hazard and signal the pipeline flush module to flush the pipeline.

 The third set of tests focused on structural hazards, where multiple instructions try to access the same resource at the same time. To simulate this, a series of instructions were loaded into the pipeline, where two instructions tried to access the memory at the same time. The hazard detection unit was expected to detect this hazard and stall the pipeline until the memory access was completed.




The above figure shows the testing for stalling and flushing.

Task 4 - Performance comparison

 Task 4 not implemented due to time constraints

Results:

- Passed 1,2,3,4,5,6,7,8 in the data memory for sorting to be applied on them
- If the sorting works properly it should be sorted as 8,7,6,5,4,3,2,1



Note: To revert to EPWave opening in a new browser window, set that option on your user page.

Sorting in working condition on pipelined processor

Flush and stall also working as can be seen from signals generated

EDA link for detailed wave: <https://www.edaplayground.com/x/AU4D>

Challenges:

The project posed several challenges that needed to be addressed to achieve the primary objective. The following are some of the challenges encountered during the project:

1. **Pipelining the Processor:** Converting the existing single-cycle processor to a pipelined one was one of the major challenges in this project. Pipelining required careful consideration of the hardware design, and various stages had to be implemented to allow for the proper flow of instructions.
3. **Hazards and their Detection:** The detection of hazards, such as data, control, and structural hazards, was another significant challenge in this project. These hazards can cause delays or incorrect execution of instructions in the pipeline, leading to incorrect results.
4. **Testing and Debugging:** Testing and debugging were essential to ensure the proper functioning of the processor. Different types of instructions had to be tested with various test cases to identify any errors and ensure that the processor could execute them correctly.
5. **Time Management:** Completing the project within the given timeline was also a challenge. The project involved several complex tasks that required careful planning and execution. Managing time efficiently was critical to ensure that the project was completed within the deadline.
6. **Implementing Sorting Algorithm:** Implementing a sorting algorithm was another significant challenge as the project required the conversion of pseudocode into assembly language using the RISC-V instruction set. Additionally, the sorting algorithm needed to be thoroughly tested to ensure that it was executing correctly on the pipelined processor.

Task Divison:

1. Task 1 - Huzaifa Riaz
2. Task 2 - Humayun Hasan
3. Task 3 - Mohammed Haider Abbas

Conclusion:

Although the project was challenging not only theoretically but the time frame which was given to complete the project was a challenge in itself. Overall, this project has helped us enhance our skills in digital design, processor architecture, pipelining, and testing, making us better equipped to take on more complex projects in the future.

Appendices:

Link to EDA Playground for Task 1: <https://www.edaplayground.com/x/wdjz>

Link to EDA Playground for Task 2 and 3 : <https://www.edaplayground.com/x/AU4D>